

TRAFFIC LIGHT CONTROLLER- Using Spartan 3E FPGA Board

PROJECT REPORT

Submitted for the course:

EEE4019: Advanced Digital Design with FPGAs

PRERNA SARKAR

16BEE0132

PAVAN KUMAR G.N.

16BEI0076



VIT[®]
Vellore Institute of Technology
(Deemed to be University under section 3 of UGC Act, 1956)

November 2019

SCHOOL OF ELECTRICAL ENGINEERING

VELLORE INSTITUTE OF TECHNOLOGY


VELLORE 632014

OBJECTIVE: To implement a Traffic Light Controller for a junction using Xilinx software for Verilog coding and FPGA Board

ABSTRACT

Traffic light controller (TLC) is used to lessen or eliminate conflicts at area shared among multiple traffic streams called intersections; by controlling the access to the intersections and apportioning effective period of time between various users. The main goal of this project is to manage the traffic movement of four intersecting roads and to achieve optimum use of the traffic. In general, traffic lights of all main roads are controlled with a fix-time system while the smaller roads are controlled autonomously by sensors.


The Traffic Light Controller is designed to generate a sequence of digital data called switching sequences that can be used to control the traffic lights of a main road and cross road junction in a fixed sequence. It plays a very important role in modern management and control of urban traffic when it comes to reducing the accident and traffic jam on roads. It is a sequential machine which needs to be analysed and programmed through a multistep process. The device involves itself in an analysis of existing sequential machines in traffic lights controllers, timing, synchronization and overview of operation and flashing light synthesis sequence. The procedure that is used in this project is designing the circuit, writing a code, simulation, synthesis and implementation in hardware. In this project, XILINX Software has been chosen to write a code using Verilog HDL (Hardware Description Language) text editor and implementation is done using Spartan 3E FPGA Board

 

THEORY

Sequential Circuits:

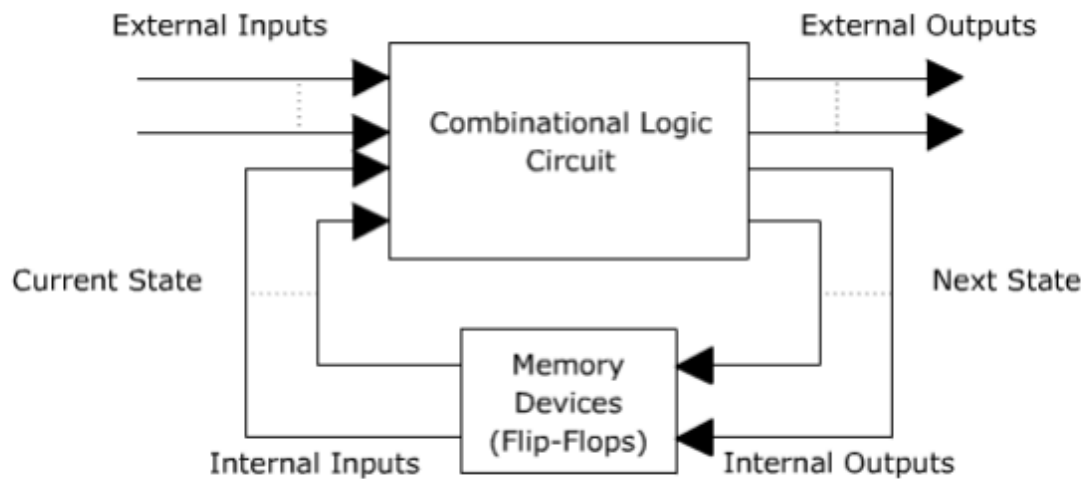
Sequential circuits work on a clock cycle which may be synchronous or asynchronous. The figure shows a basic diagram of sequential circuits. Sequential circuits use current inputs and previous inputs by storing the information and putting back into the circuit on the next clock cycle.



Finite State Machine (FSM):


A FSM is a model used to design sequential logic circuits. It is conceived as an abstract machine that can be in one of a finite number of states. The machine is in only one state at a time; the state it is in at any given time is called the current state. It can change from one state to another when initiated by a triggering event or condition, this is called a transition. A particular FSM is defined by a list of its states, and the triggering condition for each transition. This can be shown with the help of a state diagram.

ALGORITHM AND STATE DIAGRAM

 

There are two timers a long timer for green signal and a short timer for yellow signal.

State Diagram:

 

State 1: In this state, Main Road signal is green, long timer is on and Cross road signal is red. Let this state be called “MG”. When the vehicle sensor is high and the long timer is out, it goes into state 2 and long timer is reset otherwise the system remains in this state.

State 2: In this state, Main Road signal is yellow, short timer is on and Cross Road signal is red. Let this state be called “MY”. When the short timer is out, it goes into state 3 and short timer is reset, otherwise the system remains in this state.

State 3: In this state, Cross Road signal is green, long timer is on and Main Road signal is red. Let this state be called “CG”. When the long timer is out, it goes into state 4 and long timer is reset otherwise the system remains in this state.

State 4: In this state, Cross Road signal is yellow, short timer is on and Main Road signal is red. Let this state be called “CY”. When the short timer is out, it goes into state 1 and short timer is reset, otherwise the system remains in this state.

State Table:

Inputs			Present State	Next State	Outputs		
C (sensor/detector)	TL (long time pulse)	TS (short time pulse)			ST (set signal)	Main Road	Cross Road
0	-	-	MG	MG	0	Green	Red
-	0	-	MG	MG	0	Green	Red
1	1	-	MG	MY	1	Green	Red
-	-	0	MY	MY	0	Yellow	Red
-	-	1	MY	CG	1	Yellow	Red
1	0	-	CG	CG	0	Red	Green
0	-	-	CG	CY	1	Red	Green
-	1	-	CG	CY	1	Red	Green
-	-	0	CY	CY	0	Red	Yellow
-	-	1	CY	MG	1	Red	Yellow

SA1: MG = 00 MY = 01 CG = 11 CY = 10

SA2: MG = 00 MY = 10 CG = 01 CY = 11

SA3: MG = 0001 MY = 0010 CG = 0100 CY = 1000

Detectors C sense the presence of cars waiting on the cross road – with no car on cross road, light remains green in main road direction – if vehicle on cross road, main road lights go from Green to Yellow to Red, allowing the cross road lights to become green – these stay green only as long as a cross road car is detected but never longer than a set interval; after the interval expires, cross lights transition from Green to Yellow to Red, allowing main road to return to green – even if cross road vehicles are waiting, main road gets at least a set interval of green

Assume you have an interval timer that generates: – a short time pulse (TS) and – a long time pulse (TL), – in response to a set (ST) signal. – TS is to be used for timing yellow lights and TL for green lights

CODE

- Main Code: traffic_light.v

```
`timescale 1ns / 1ps

module traffic_light(light_main, light_cross, C, clk, rst_n, mr, my, mg, cr, cy, cg);

parameter MGRE_CRED=2'b00, // main green and cross red

    MYEL_CRED = 2'b01, // main yellow and cross red

    MRED_CGRE=2'b10, // main red and cross green

    MRED_CYEL=2'b11; // main red and cross yellow

input C, // sensor

    clk, // clock = 50 MHz

    rst_n; // reset active low

output reg[2:0] light_main, light_cross; // output of lights

output reg mr, my, mg, cr, cy, cg;

reg[27:0] count=0, count_delay=0;

reg delay10s=0,
    delay3s1=0, delay3s2=0, RED_count_en=0, YELLOW_count_en1=0, YELLOW_count_en2=0;

wire clk_enable; // clock enable signal for 1s

reg[1:0] state, next_state;

// next state

always @(posedge clk or negedge rst_n)

begin

if(~rst_n)

state <= 2'b00;
```

```

else

    state <= next_state;

end

// FSM

always @(*)

begin

    case(state)

    MGRE_CRED: begin // Green on main and red on cross way

        RED_count_en=0;

        YELLOW_count_en1=0;

        YELLOW_count_en2=0;

        light_main = 3'b001;

        light_cross = 3'b100;

        mr = 1'b0;

        my = 1'b0;

        mg = 1'b1;

        cr = 1'b1;

        cy = 1'b0;

        cg = 1'b0;

        if(C) next_state = MYEL_CRED;

        // if sensor detects vehicles on cross road,

        // turn main to yellow -> green

    else next_state =MGRE_CRED;

    end

    MYEL_CRED: begin// yellow on main and red on cross way

        light_main = 3'b010;

```



```
light_cross = 3'b100;

RED_count_en=0;

YELLOW_count_en1=1;

YELLOW_count_en2=0;

mr = 1'b0;

my = 1'b1;

mg = 1'b0;

cr = 1'b1;

cy = 1'b0;

cg = 1'b0;

if(delay3s1) next_state = MRED_CGRE;

// yellow for 3s, then red

else next_state = MYEL_CRED;

end

MRED_CGRE: begin// red on main and green on cross way

light_main = 3'b100;

light_cross = 3'b001;

RED_count_en=1;

YELLOW_count_en1=0;

YELLOW_count_en2=0;

mr = 1'b1;

my = 1'b0;

mg = 1'b0;

cr = 1'b0;

cy = 1'b0;

cg = 1'b1;
```

```

if(delay10s) next_state = MRED_CYEL;

// red in 10s then turn to yello -> green again for high way

else next_state =MRED_CGRE;

end

MRED_CYEL:begin// red on main and yellow on cross way

light_main = 3'b100;

light_cross = 3'b010;

RED_count_en=0;

YELLOW_count_en1=0;

YELLOW_count_en2=1;

mr = 1'b1;

my = 1'b0;

mg = 1'b0;

cr = 1'b0;

cy = 1'b1;

cg = 1'b0;

if(delay3s2) next_state = MGRE_CRED;

// turn green for main, red for cross road

else next_state =MRED_CYEL;

end

default: next_state = MGRE_CRED;

endcase

end

// create red and yellow delay counts

always @(posedge clk)

```

```
begin

if(clk_enable==1) begin

if(RED_count_en||YELLOW_count_en1||YELLOW_count_en2)

count_delay <=count_delay + 1;

if((count_delay == 9)&&RED_count_en)

begin

delay10s=1;

delay3s1=0;

delay3s2=0;

count_delay<=0;

end

else if((count_delay == 2)&&YELLOW_count_en1)

begin

delay10s=0;

delay3s1=1;

delay3s2=0;

count_delay<=0;

end

else if((count_delay == 2)&&YELLOW_count_en2)

begin

delay10s=0;

delay3s1=0;

delay3s2=1;

count_delay<=0;

end

else
```

```

begin

delay10s=0;

delay3s1=0;

delay3s2=0;

end

end

end

// create 1s clock enable

always @(posedge clk)

begin

count <=count + 1;

//if(count == 50000000) // 50,000,000 for 50 MHz clock running on real FPGA

if(count == 3) // for testbench

count <= 0;

end

assign clk_enable = count==3 ? 1: 0; // 50,000,000 for 50MHz running on FPGA

endmodule

```

- **Test Bench: tb_traffic.v**

```

timescale 1ns / 1ps

//^timescale 10 ns/ 1 ps

`define DELAY 1

//include "counter_define.h"

module tb_traffic;

parameter ENDTIME = 400000;

//integer count, count1, a;

```

```
reg clk;

reg rst_n;

reg C;

wire [2:0] light_cross;

wire [2:0] light_main;


traffic_light tb(light_main, light_cross, C, clk, rst_n);


initial

begin

clk = 1'b0;

rst_n = 1'b0;

C = 1'b0;

//count = 0;

//count1=0;

//a=0;

end

initial

begin

main;

end

task main;

fork

clock_gen;

reset_gen;

operation_flow;
```

```
debug_output;  
  
endsimulation;  
  
join  
  
endtask  
  
task clock_gen;  
  
begin  
  
forever #`DELAY clk = !clk;  
  
end  
  
endtask
```

```
task reset_gen;  
  
begin  
  
rst_n = 0;  
  
# 20  
  
rst_n = 1;  
  
end  
  
endtask
```

```
task operation_flow;  
  
begin  
  
# 19  
  
C = 0;  
  
# 17  
  
C = 1;  
  
# 16  
  
C = 0;
```

```
# 19
```

```
C = 1;
```

```
end
```

```
endtask
```

```
task debug_output;
```

```
begin
```

```
$monitor("TIME = %d, reset = %b, C = %b, light of main = %h, light of cross road =  
%h",$time,rst_n,C,light_main,light_cross );
```

```
end
```

```
endtask
```

```
task endsimulation;
```

```
begin
```

```
#ENDTIME
```

```
$display("----- THE SIMUALTION END -----");
```

```
$finish;
```

```
end
```

```
endtask
```

```
endmodule
```

- **UCF File: traffic_light.ucf**

clock signal for 50 MHz

NET "clk" LOC = C9 | IOSTANDARD = LVCMOS33;

NET "clk" PERIOD = 20.0ns HIGH 50%;

#input for switch

NET "C" LOC = "L13" | IOSTANDARD = LVTTTL | PULLUP ;

output for LED

NET "mr" LOC = "F9" | IOSTANDARD = LVTTTL | SLEW = SLOW | DRIVE = 8 ; // Main road red

NET "my" LOC = "E9" | IOSTANDARD = LVTTTL | SLEW = SLOW | DRIVE = 8 ; // main road
yellow



NET "mg" LOC = "D11" | IOSTANDARD = LVTTTL | SLEW = SLOW | DRIVE = 8 ; // main road
green

NET "cr" LOC = "E11" | IOSTANDARD = LVTTTL | SLEW = SLOW | DRIVE = 8 ; // cross road
red

NET "cy" LOC = "E12" | IOSTANDARD = LVTTTL | SLEW = SLOW | DRIVE = 8 ; // cross road
yellow

NET "cg" LOC = "F12" | IOSTANDARD = LVTTTL | SLEW = SLOW | DRIVE = 8 ; // cross road
green

OUTPUT

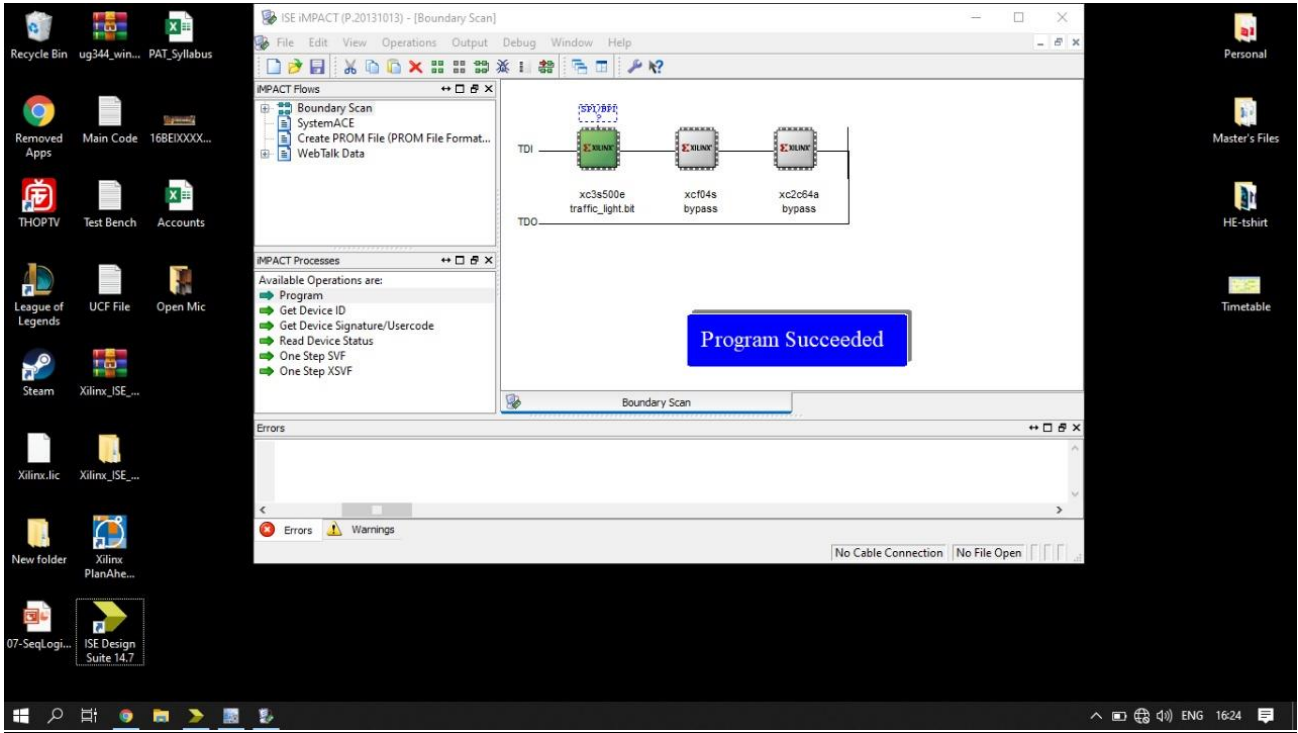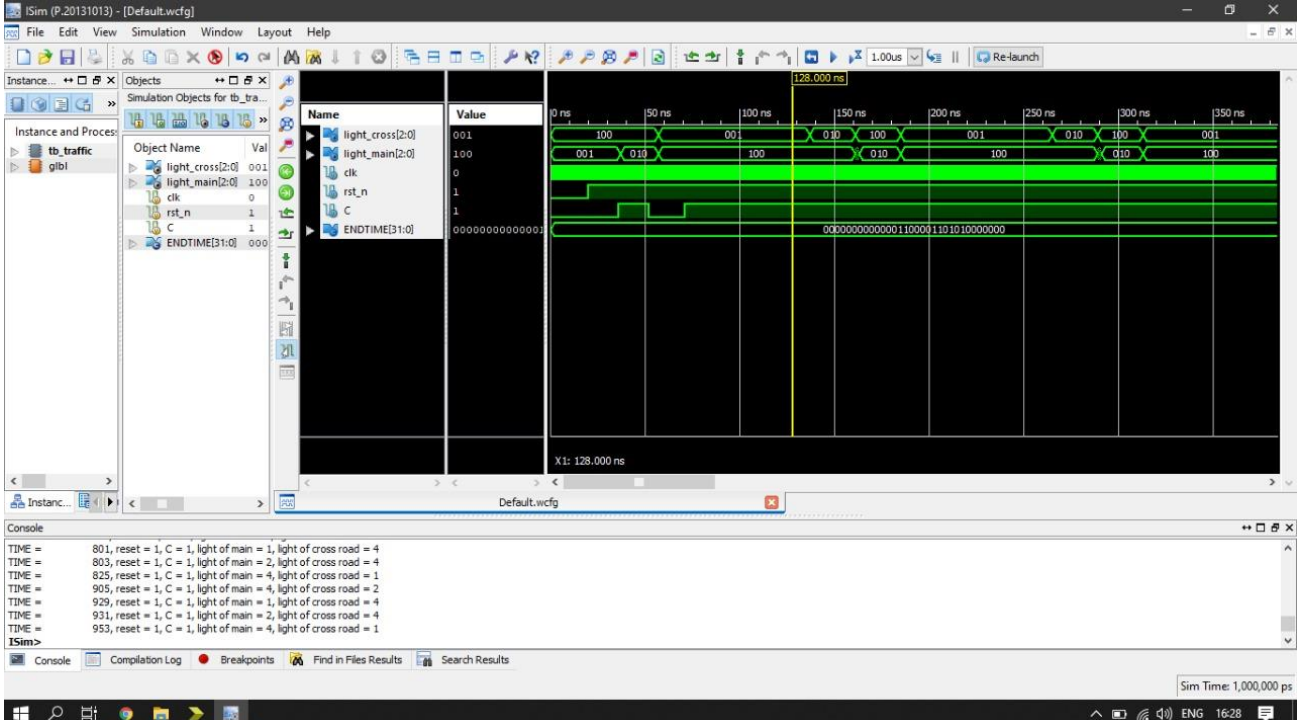

REFERENCES

- El-Medany, W. M., & Hussain, M. R. (2007, September). FPGA-based advanced real traffic light controller system design. In *2007 4th IEEE Workshop on Intelligent Data Acquisition and Advanced Computing Systems: Technology and Applications* (pp. 100-105). IEEE.
- Chavan, S. S., Deshpande, R. S., & Rana, J. G. (2009, December). Design of intelligent traffic light controller using embedded system. In *2009 Second International Conference on Emerging Trends in Engineering & Technology* (pp. 1086-1091). IEEE.
- Han, T., & Lin, C. (2002, October). Design of an intelligence traffic light controller (ITLC) with VHDL. In *2002 IEEE Region 10 Conference on Computers, Communications, Control and Power Engineering. TENCOM'02. Proceedings.* (Vol. 3, pp. 1749-1752). IEEE.